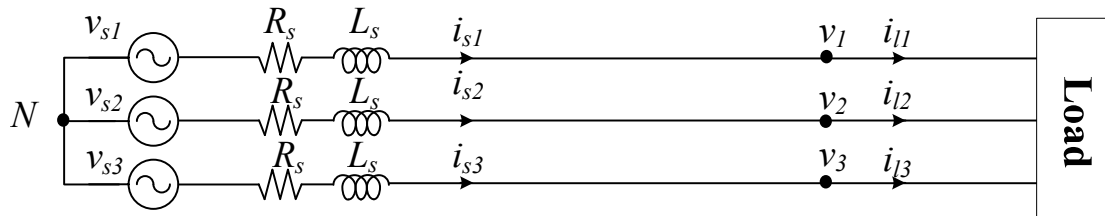


Simulation Assignment


Q1: Draw V_α , V_β , V_d , and V_q from the load voltage (v_1 , v_2 , and v_3) in the following figure:



Note 1: The grid voltages and load are balanced.

Note 2: Feel free to select any values for the voltage and parameters.

SIMULINK Figure:

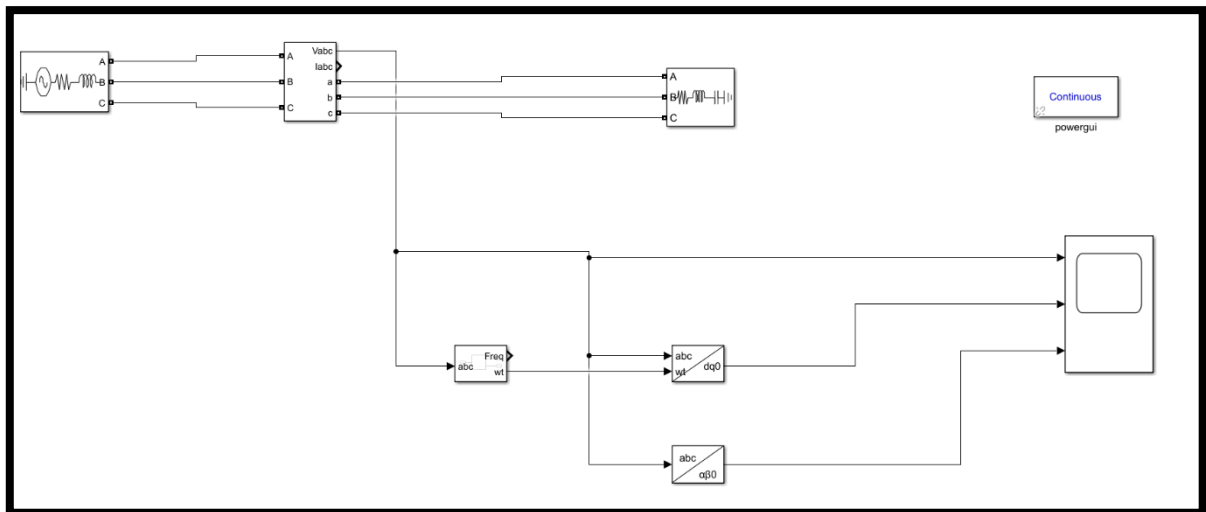

The model here represents a 3-Phase AC Voltage Source, 3-Phase Voltage Measurement Block, 3-Phase RLC Load, V_{abc} to V_{dq} Conversion Block and V_{abc} to $V_{\alpha\beta}$ Conversion Block. The results are then plotted using the Scope block which can be seen below. This figure is a representation of Park Transformation.

Voltage Waveforms:

